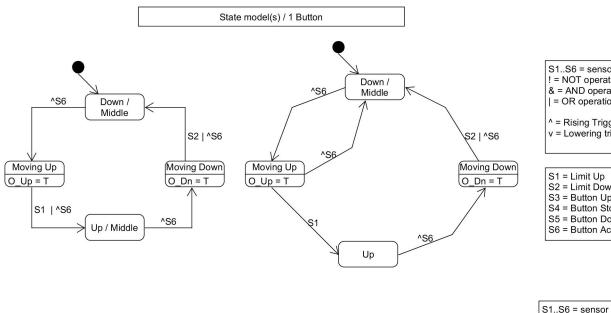


S1..S6 = sensor
! = NOT operation
& = AND operation
| = OR operation
^ = Rising Trigger
v = Lowering trigger


S1 = Limit Up S2 = Limit Down S3 = Button Up S4 = Button Stop

S5 = Button Down S6 = Button Activate (One button operation)



S1..S6 = sensor
! = NOT operation
& = AND operation
| = OR operation
^ = Rising Trigger
v = Lowering trigger
v = Lowering trigger

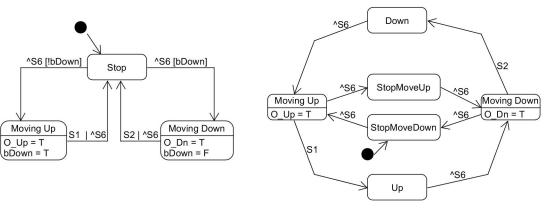S1 = Limit Up
S2 = Limit Down
S3 = Button Up
S4 = Button Stop
S5 = Button Down
S6 = Button Activate (One button operation)



! = NOT operation & = AND operation | = OR operation | - Rising Trigger v = Lowering trigger

S1 = Limit Up
S2 = Limit Down
S3 = Button Up
S4 = Button Stop
S5 = Button Down
S6 = Button Activate (One button operation)